

Name: Tausid Chowdhury ID: 22101182 Sec: 17 Group: 03 Date: 06/02/23

Experiment no: 04

Name of the Experiment: Determination of the resistance of a galvanometer by half deflection method.


Questions on theory (all diagrams should be drawn by using a pencil and a scale)

*1) What is resistance of the galvanometer? [0.25]

Ans: Resistance of galvanometer is the resistance of a coil of wire wound over a rectangular frame kept in a magnetic field inside the galvanometer.

*2) Draw the circuit diagram for this experiment. [0.25]

Ans:

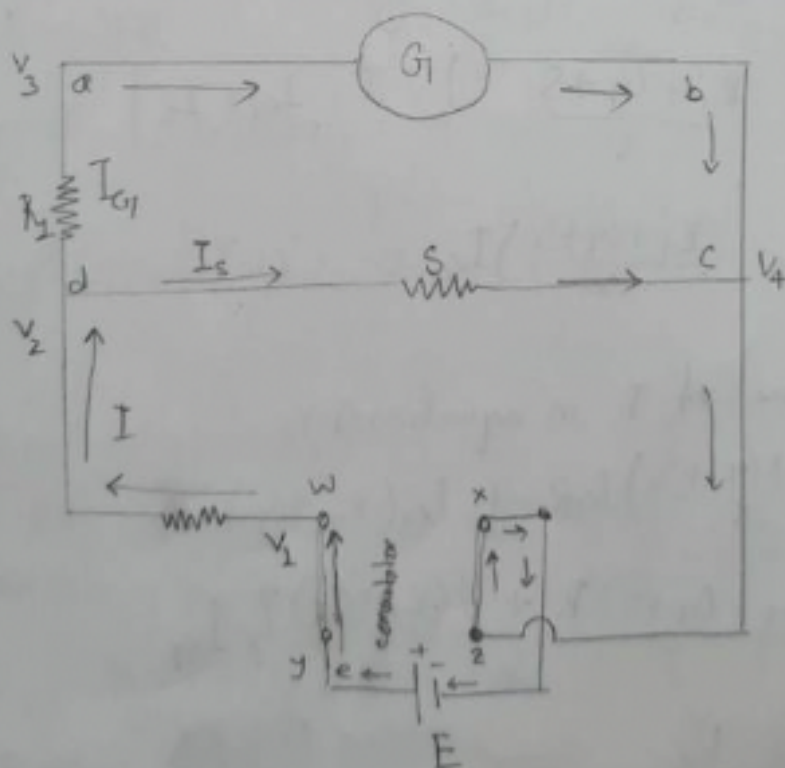

*3) Derive an expression for the current passing through the galvanometer as a function of the resistances of the shunt box, two resistance boxes and the emf of the voltage source, i.e., equation (8). [2]

Ans: Using Kirchhoff's loop voltage rule in the circuit diagram's adabcde loop,

$$IR + I_G R_1 + I_G G_1 - E = 0$$

$$\Rightarrow E = IR + I_G (R_1 + G_1) \dots (i)$$

Using Kirchhoff's loop voltage rule in closed loop abcda,

$$I_G R_1 + I_G G_1 - I_s S = 0$$

$$\Rightarrow I_s S = I_G (R_1 + G_1)$$

$$\Rightarrow \frac{I_s}{I_G} = \frac{R_1 + G_1}{S}$$

$$\Rightarrow \frac{I_s + I_G}{I_G} = \frac{R_1 + G_1 + S}{S}$$

$$\Rightarrow \frac{I}{I_G} = \frac{R_1 + G_1 + S}{S} \quad [\because I = I_G + I_s]$$

$$\therefore I = \left(\frac{R_1 + G_1 + S}{S} \right) I_G \dots (ii)$$

Plugging in the value of I in equation (i):

$$E = \left(\frac{R_1 + G_1 + S}{S} \right) I_G R + I_G (R_1 + G_1)$$

$$= \left\{ \frac{(R_1 + G_1 + S) R + S (R_1 + G_1)}{S} \right\} I_G$$

$$I_G = \frac{E S}{(R_1 + G_1 + S) R + S (R_1 + G_1)}$$

*4) Show that, the value of R_1 for which the galvanometer's deflection is reduced down to the half of the deflection when $R_1 = 0$, is approximately equal to the galvanometer's resistance. [2]

Ans: We know,

Deflection angle of the galvanometer's pointer θ is proportional to the current passing through the galvanometer, I_G

$$\therefore \theta \propto I_G$$

$$\Rightarrow \theta = \frac{1}{K} I$$

$$I_G = K\theta \quad [K = \text{Galvanometer's constant}]$$

$$\text{If } R_1 = 0$$

$$\frac{E_S}{R_G + R_S + G_S} = K\theta \quad \dots \dots (i)$$

When Galvanometer's deflection is reduced down to the half deflection

$$\frac{E_S}{(R_1 + G + S)R + S(R_1 + G)} = \frac{K\theta}{2} \quad \dots \dots (ii)$$

$$(i) \div (ii) \Rightarrow$$

$$\frac{R + G + S}{(R_1 + G + S)R + S(R_1 + G)} = 2$$

$$\Rightarrow \frac{R + G + S}{(R_1 + G + S)R + S(R_1 + G)} = 2$$

$$\Rightarrow 1 + \frac{R R_1 + R_1 S}{R G + R S + G S} = 2$$

As S is very much smaller than R and G we can neglect the terms containing S in the equation

$$\therefore R \approx G$$

5) For a certain value of shunt-resistance, θ and deflection of the galvanometer is shown in Figure A.



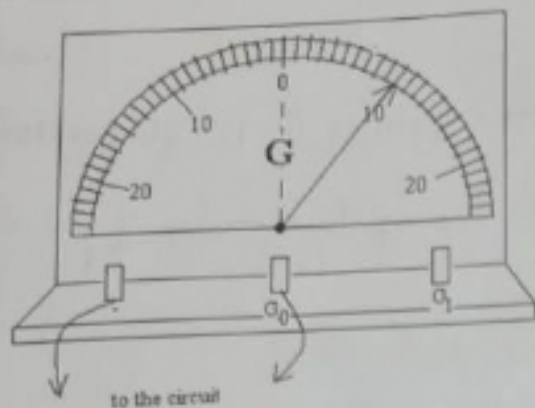


Figure A: Deflection when $R_1 = 0$

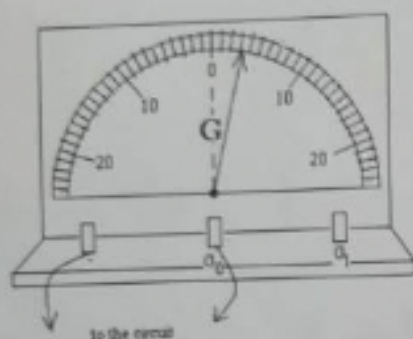
By keeping S and R fixed the deflections of the galvanometer for different values of R_1 are shown in the following figures.



when $R_1 = 6 \Omega$

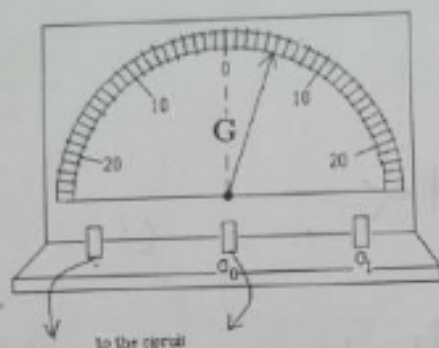

when $R_1 = 3 \Omega$

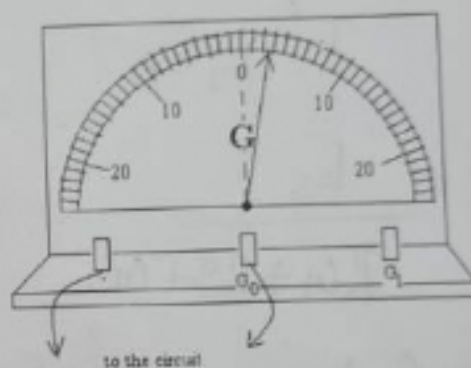

when $R_1 = 9 \Omega$

What is the internal resistance of the galvanometer? [0.5]

Ans: $R_1 = 6 \Omega$

$$1 + R/G = \frac{\theta_1}{\theta_2} \text{ deflection}$$

$$1 + R/G = \frac{10}{3}$$

$$\Rightarrow \frac{6}{G} = \frac{7}{3}$$

$$\Rightarrow G = \frac{6 \times 3}{7}$$

$$\therefore G = 2.57 \Omega$$

when $R_1 = 3 \Omega$,

$$1 + R/G = 10/5$$

$$\therefore R/G = 1 \Rightarrow R = G = 3 \Omega$$

when $R_1 = 9 \Omega$

$$1 + R/G = \frac{10}{2.5}$$

$$R/G = 4.1$$

$$G = 3 \Omega$$

$$\therefore \text{internal resistance} = \frac{3 + 3 + 2.57}{3}$$

$$= 2.92 \Omega$$

$$\approx 3 \Omega$$

- Draw the data table(s) and write down the variables to be measured shown below (in the 'Data' section), using pencil and ruler BEFORE you go to the lab class.
- Write down your NAME and ID on the top of the page.
- This part should be separated from your Answers of "Questions on Theory" part.
- Keep it with yourself after coming to the lab.

Data

Table: Data for determining the resistance of a galvanometer

No. of observation	R (Ω)	S (Ω)	Flow of current	Deflection when $R_1=0$ (θ_0)	$R_1 (\neq 0)$ (Ω)	Deflection when $R_1 \neq 0$ (θ)	G $= R_1 / \left(\frac{\theta_0}{\theta} - 1 \right)$ (Ω)	Mean G (Ω)
1	50	-2	D	43	100	21.5	100	110.833
			L	43	120	15.2	120	
2	20	.2	D	8	140	4	140	
			L	8	140	4.5	140	
3	20	.3	D	12	120	6	120	
			L	10	100	5	100	
4	50	.3	D	4	120	2	120	
			L	6	110	3	110	
5	30	.2	D	5	110	2.5	110	
			L	5	70	2.5	70	
6	30	.3	D	6	100	3	100	
			L	6	100	3	100	

- READ the PROCEDURE carefully and perform the experiment by YOURSELVES. If you need help to understand any specific point draw attention of the instructors.
- DO NOT PLAGIARIZE data from other group and/or DO NOT hand in your data to other group. It will bring ZERO mark in this experiment. Repetition of such activities will bring zero mark for the whole lab.
- Perform calculations by following the PROCEDURE . Show every step in the Calculations section.
- Write down the final result(s)

Calculations

Results: